







. Resistance: the property of a conductor to resist the flow of charge through it

- Factors effecting Resistance

- 1. Length ---> Length Resistance (More collision of electrons)
- 2. Area of cross-section --> Area¹ Resistance (Less collision of electrons)
- 3. Temperature -> Temperature ? Resistance ?
- 4. Nature of material

→Increase movement of e⁻ and K.E

Resistivity/Specific resistance

RKL	P= mho/ohm
$R \propto \frac{1}{2}$	$\Omega = 1 \frac{m}{m}$
RØL	m ²
Ā	
$R = \frac{PL}{A}$	3.1 UN

The resistivity of a material is the resistance of a wire of that material



	Material	Resistivity (Ω m)
Conductors	Silver	1.60×10^{-8}
	Copper	1.62×10^{-8}
	Aluminium	2.63×10^{-8}
	Tungsten	5.20×10^{-8}
	Nickel	6.84×10^{-8}
	Iron	10.0×10^{-8}
	Chromium	12.9×10^{-8}
	Mercury	94.0×10^{-8}
	Manganese	1.84×10^{-6}
Alloys	Constantan	49×10^{-6}
	(alloy of Cu and Ni)	
	Manganin	44×10^{-6}
/	(alloy of Cu, Mn and Ni)	
/	Nichrome	100×10^{-6}
1	(alloy of Ni, Cr, Mn and Fe)	
Insulators	Glass	$10^{10} - 10^{14}$
	Hard rubber	$10^{13} - 10^{16}$
	Ebonite	$10^{15} - 10^{17}$
X	Diamond	$10^{12} - 10^{13}$
	Paper (drv)	1012
	1	

Alloy has greater resistivity than its constituent metals

Types of Materials

• Conductor: materials that conduct electricity/allow electric flow through them -> Has free electrons Seen in metals

- Semi-conductor: they are materials which have conductivity between conductors and nonconductors or insulator. Eg: Silicon (usually Metalloids)
- Insulator: materials that do not allow electricity to pass through them. Eg: Non-metals such as glass, wood





· Series: same current; different potential difference

· Parallel: same potential difference; different current

Q. 2 resistors = 20Ω and 4Ω (Series) Connected to a 6 volt battery Current flow?

۷	=	IR
۷	=	IR

$$R_{eq} = R_1 + R_2$$
20 + 4 = 24.2
6 V = 1 x 24.2
1 $\frac{6}{24}$ = 1
4 $\frac{24}{24}$
0.25 A = 1

Q. $R_1 = 5_{\Omega}$; $R_2 = 10_{\Omega}$; $R_3 = 30_{\Omega}$ \longrightarrow Parallelly connected P.d = 12 V Current?

.

V = 12 <u>12</u> 5 2.4	IR = 1 x 5 = 1 A = 1	V = IR 12 = I x 10 1.2 A = I → 2.4 + 1.2	V = IR 12 = I x 3 0.4 A = I + 0.4 = 4.0 A	0
	OR →	$\frac{1}{R_{eq}} = \frac{1}{R_{i}} + \frac{1}{2}$ $\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{2}$ $\frac{1}{R_{eq}} = \frac{1}{30}$ $\frac{1}{R_{eq}} = \frac{10}{30}$ $R = 3 \text{ p}$	$\frac{1}{R_2} + \frac{1}{R_3}$ $\frac{+1}{30}$ $+ \frac{1}{1}$	V = IR 12 = x <i>3</i> = <mark>4 A</mark>



Heating effect of Electric Current



Practical Applications of Heating Effect of Electric Current





P = VI $P = I^{2}R \quad V = IR$ $P = V^{2} \quad V = I$ $R \quad V = I$

Commercial Unit of Energy 1 unit = 1 kWh P x t 1 kW = 1000 W

1 hr = 60 mins 60 x 60 = 3600 secs

Colour of wire

- 220 V; 50 Hz ---> In electric appliances
- Live wire: Red

• Neutral: Black

·Ground/Earth: Green/Yellow